
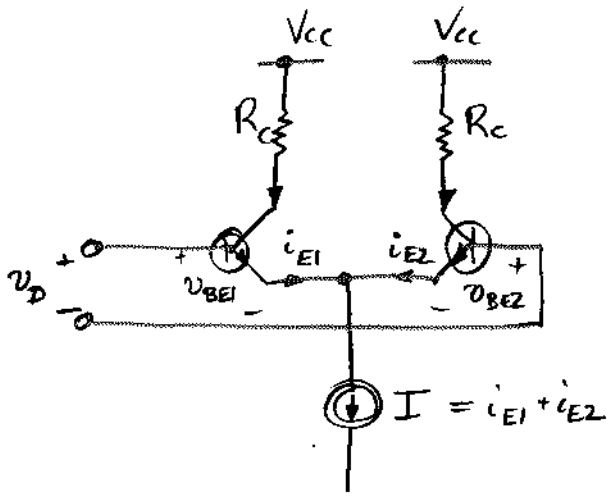


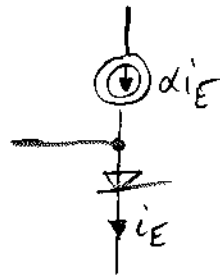LARGE-SIGNAL OPERATION OF THE BJT DIFF. PAIR



using the T model.



$$i_{E1} = I_{SE} e^{\frac{v_{BE1}}{V_T}}$$

$$i_{E2} = I_{SE} e^{\frac{v_{BE2}}{V_T}}$$

"-" $i_{E1} - i_{E2} = I_{SE} \left(e^{\frac{v_{BE1}}{V_T}} - e^{\frac{v_{BE2}}{V_T}} \right)$

"+" $i_{E1} + i_{E2} = I_{SE} \left(e^{\frac{v_{BE1}}{V_T}} + e^{\frac{v_{BE2}}{V_T}} \right)$

Note:


$$\frac{e^x - e^y}{e^x + e^y} = \frac{e^{\frac{-x-y}{2}}}{e^{\frac{x-y}{2}}} \frac{e^x - e^y}{e^x + e^y} =$$

$$\frac{e^{\frac{x-y}{2}} - e^{-\frac{x-y}{2}}}{e^{\frac{x-y}{2}} + e^{-\frac{x-y}{2}}} = \tanh \frac{x-y}{2}$$

$$\frac{i_{E1} - i_{E2}}{i_{E1} + i_{E2}} = \tanh \frac{v_{BE1} - v_{BE2}}{2V_T}$$

$$i_{E1} - i_{E2} = I \tanh \frac{v_D}{2V_T}$$


$$\left. \frac{d(i_{E1} - i_{E2})}{dv_D} \right|_{v_D=0} = \frac{I}{2V_T} = \frac{1}{r_e}$$

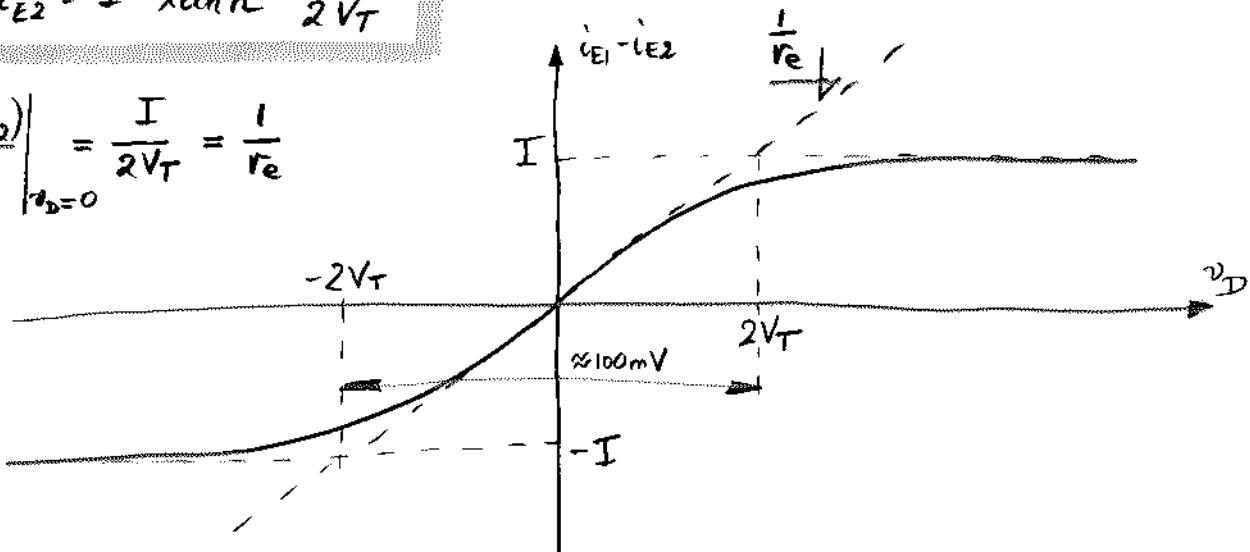

or

$$\left. \frac{d(i_{E1} - i_{E2})}{dv_D} \right|_{v_D=0} = \frac{\alpha}{r_e} = g_m$$

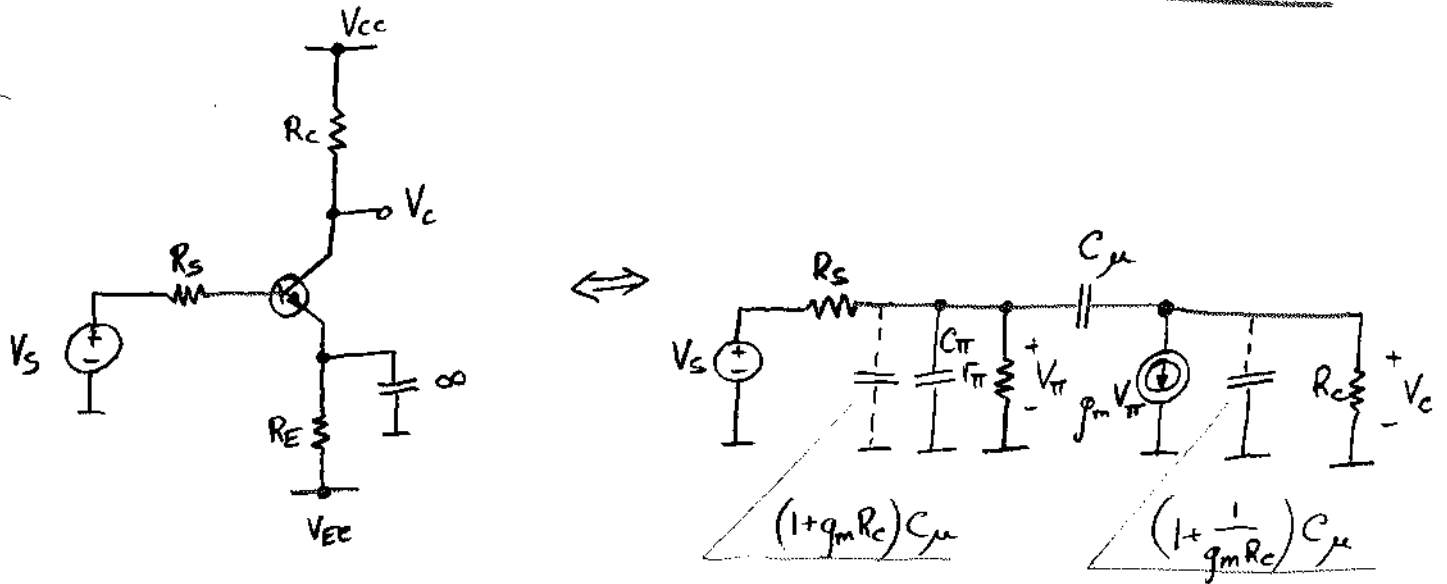HIGH FREQUENCY RESPONSE OF A CE AMPLIFIER (BJT)



Mid-band voltage gain:

$$V_{\pi} = V_c \frac{r_{\pi}}{R_s + r_{\pi}}, \quad V_c = -g_m V_{\pi} \cdot R_c = -\frac{r_{\pi}}{R_s + r_{\pi}} g_m R_c V_s = -\underbrace{\frac{R_s \parallel r_{\pi}}{R_s}}_{\frac{1}{a}} \underbrace{g_m R_c}_A V_s$$

High freq. response:

$$f_{H1} = \frac{1}{2\pi (R_s \parallel r_{\pi}) [(1+g_m R_c) C_{\mu} + C_{\pi}]}$$


$$f_{H2} = \frac{1}{2\pi R_c (1 + \frac{1}{g_m R_c}) C_{\mu}}$$

$$f_H = \frac{f_{H1} f_{H2}}{f_{H1} + f_{H2}}$$

Gain-bandwidth product:

$$\begin{aligned} \frac{1}{A_{vo} 2\pi f_H} &= \left[(R_s \parallel r_{\pi}) [(1+g_m R_c) C_{\mu} + C_{\pi}] + R_c (1 + \frac{1}{g_m R_c}) C_{\mu} \right] \frac{R_s}{R_s \parallel r_{\pi}} \frac{1}{g_m R_c} = \\ &= \left(\frac{R_s}{a} [(1+A) C_{\mu} + C_{\pi}] + R_c (1 + \frac{1}{A}) C_{\mu} \right) \frac{a}{A} = \\ &= R_s (1 + \frac{1}{A}) C_{\mu} + \frac{1}{A} R_s C_{\pi} + \frac{a}{A} R_c (1 + \frac{1}{A}) C_{\mu} = \\ &= R_s C_{\mu} + \frac{1}{A} R_s (C_{\mu} + C_{\pi}) + R_c \frac{a}{A} (1 + \frac{1}{A}) C_{\mu} \\ (GB) &= \frac{1}{2\pi} \frac{1}{R_s C_{\mu} + \frac{1}{A} [R_s (C_{\mu} + C_{\pi}) + a R_c (1 + \frac{1}{A}) C_{\mu}]} \end{aligned}$$

THE COMPLETE EBERS-MOLL MODEL OF A BJT:

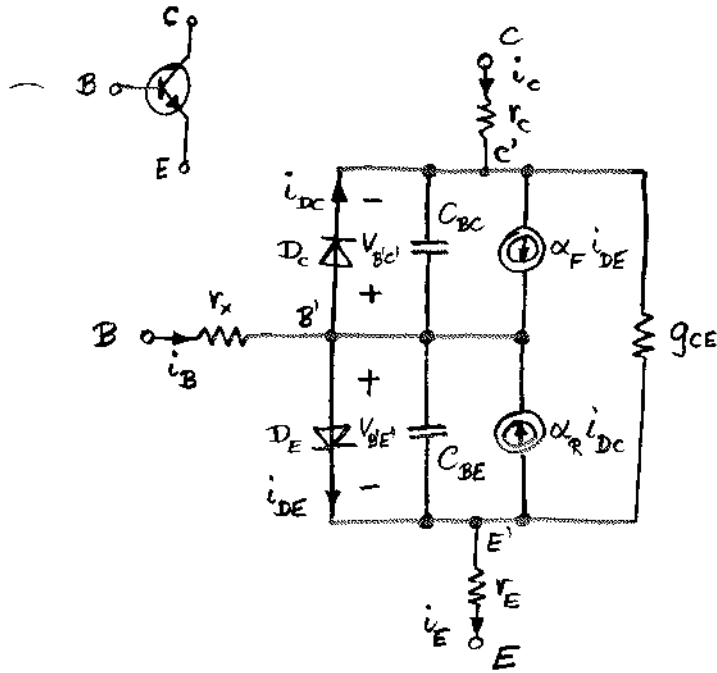

$$i_{DE} = I_{SE} \left(e^{\frac{V_{BE'}}{n_F \phi_T}} - 1 \right)$$

$$i_{DC} = I_{SC} \left(e^{\frac{V_{BC'}}{n_R \phi_T}} - 1 \right)$$

$$\text{with } g_{BE} = \frac{d i_{DE}}{d V_{BE'}} = \frac{i_{DE} + I_{SE}}{n_F \phi_T}$$

$$g_{BC} = \frac{d i_{DC}}{d V_{BC'}} = \frac{i_{DC} + I_{SC}}{n_R \phi_T}$$

$$g_{CE} = G_Z + N_G (g_{BE} + g_{BC})$$

$$C_{BE} = \alpha_F \tau_F g_{BE} + \frac{C_{je0}}{\left(1 - \frac{V_{BE'}}{V_{oe}}\right)^{m_E}}$$

$$C_{BC} = \alpha_R \tau_R g_{BC} + \frac{C_{jc0}}{\left(1 - \frac{V_{BC'}}{V_{oc}}\right)^{m_C}}$$

Example set of parameters of a BJT:

$I_{SE} = 0.02 \text{ pA}$ (emitter saturation current)

$I_{SC} = 0.0264 \text{ pA}$ (collector saturation current)

$\phi_T = \frac{kT}{q} \approx 0.026 \text{ V}$ (thermal potential of electron)

$n_F = 1$ (emitter emission coefficient)

$n_R = 1$ (collector emission coefficient)

$\alpha_F = 0.99$ (forward scale factor)

$\alpha_R = 0.75$ (reverse scale factor)

$G_Z = 0$ (Early's parameter)

$N_G = 0.00025$ (Early's parameter)

$\tau_F = 0.2 \text{ ns}$ (forward transit time)

$\tau_R = 6.3 \text{ ns}$ (reverse transit time)

$C_{je0} = 5 \text{ pF}$ (emitter junction unbiased cap)

$C_{jc0} = 4 \text{ pF}$ (collector junction unbiased cap)

$V_{oe} = 0.8 \text{ V}$ (emitter junction built-in volt.)

$V_{oc} = 0.8 \text{ V}$ (collector junction built-in volt.)

$m_E = 0.333$ (emitter Schottky's grading coeff.)

$m_C = 0.333$ (collector Schottky's grading coeff.)


$r_x = 50 \Omega$ (zero-bias base ohmic resistance)

$r_E = 0 \Omega$ (zero-bias emitter ohmic resistance)

$r_c = 0 \Omega$ (zero-bias collector ohmic resistance)

The Miller effect

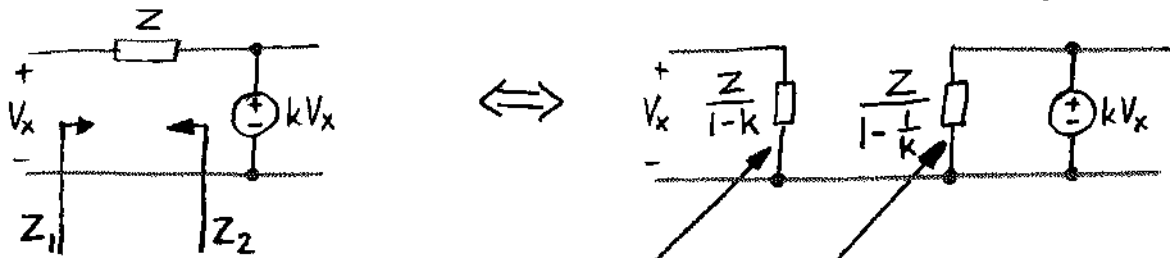
The following two circuits are equivalent:



$$Z_1 = \frac{V_x}{\frac{V_x - kV_x}{Z}} = \frac{Z}{1-k}$$

$$Z_2 = \frac{kV_x}{\frac{kV_x - V_x}{Z}} = \frac{Z}{1-\frac{1}{k}}$$

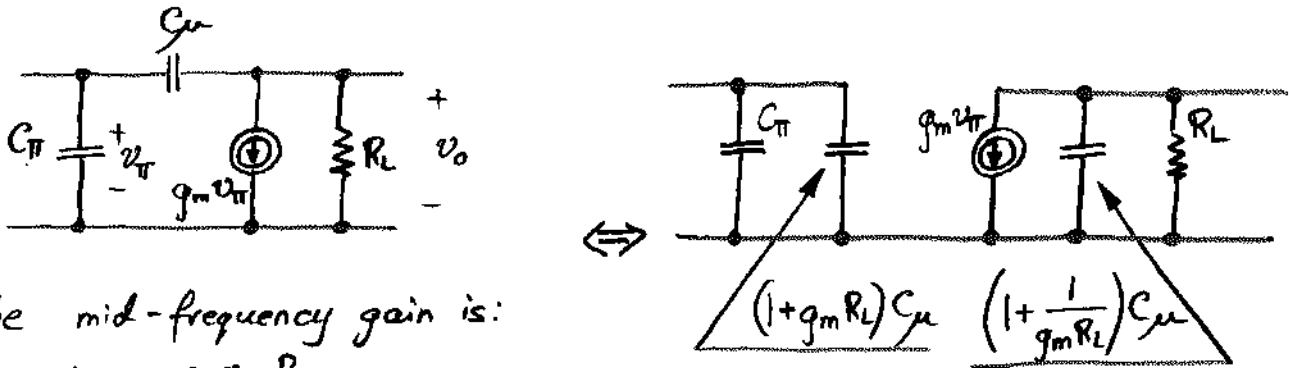This fact simplifies the analysis of transistor circuits:



The mid-frequency gain is:

$$k = \frac{v_o}{v_\pi} = \frac{-g_m v_\pi \cdot R_L}{v_\pi} = -g_m R_L$$

$$Z_\mu = \frac{1}{sC_\mu} \rightarrow Z_1 = \frac{Z_\mu}{1+g_m R_L} = \frac{1}{s(1+g_m R_L)C_\mu}$$

$$Z_2 = \frac{Z_\mu}{1+\frac{1}{g_m R_L}} = \frac{1}{s\left(1+\frac{1}{g_m R_L}\right)C_\mu}$$